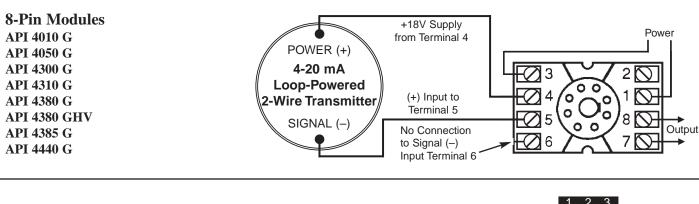


Using the Built-In 4-20 mA Loop Power Supply

Many Api modules have a built in loop power supply which can be used to power the 4-20 mA input current loop. The wiring diagrams below give examples of how a two-wire transmitter can be powered by the module's loop power supply and also provide input to the module.

When using the built-in loop power supply, there is no connection to the module's signal minus (–) input terminal. An **internal** 50 ohm resistor across the input terminals allows you to do this without any problems.




DIN Pack Modules API 1080 DIN API 1090 DIN

API 1090 DD

API 4380 DIN



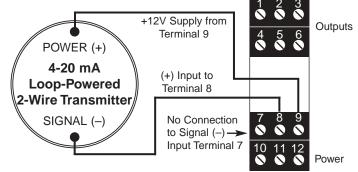

11-Pin Modules


API 1005 G

API 1025 G

API 1040 G

API 1080 G

API 1090 G

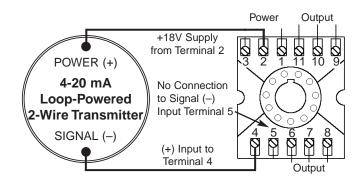

Did You Know...?

Api plug-in style modules are hot-swappable. You can change them in the field while powered up in order to minimize downtime.

FREE APPLICATION ASSISTANCE Call $\widehat{\mathcal{A}}$ η Customer Service 800-942-0315

> **G-8** Rev 04/02 APIAN055